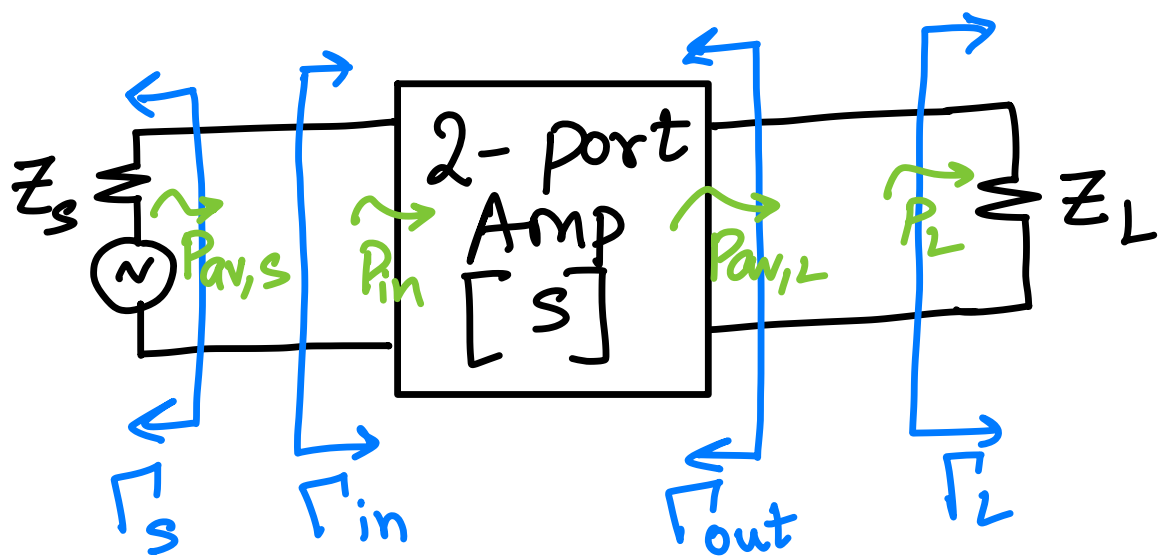




RF Amplifier



$$\Gamma_s = \frac{Z_s - Z_0}{Z_s + Z_0}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma_{in} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$

$$\Gamma_{out} = S_{22} + \frac{S_{12} S_{21} \Gamma_s}{1 - S_{11} \Gamma_s}$$

(Pozar
Sec 12.1)

$P_{av,s}$ = Power the source would deliver to a conjugate matched load (amp)

P_{in} = Actual power delivered to the load (amp)

$P_{av,L}$, P_{out} are similarly defined.

Gain definitions

$$G_T: \text{Transducer Power Gain} = \frac{P_L}{P_{av,s}} \quad \left. \vphantom{\frac{P_L}{P_{av,s}}} \right\} \text{Includes both } \Gamma_p \times \Gamma_L \text{ match}$$

$$G_P: \text{Operating Power Gain} = \frac{P_L}{P_{in}} \quad \left. \vphantom{\frac{P_L}{P_{in}}} \right\} \text{Only depends on } Z_L$$

$$G_A: \text{Available Power Gain} = \frac{P_{av,L}}{P_{av,s}} \quad \left. \vphantom{\frac{P_{av,L}}{P_{av,s}}} \right\} \text{Only depends on } Z_s.$$


$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2) (1 - |\Gamma_L|^2)}{|1 - \Gamma_s \Gamma_{in}|^2 |1 - S_{22} \Gamma_L|^2}$$

$$G_A = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)}{|1 - S_{11} \Gamma_s|^2 (1 - |\Gamma_{out}|^2)}$$

$$G_P = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2) (1 - |S_{22} \Gamma_L|^2)}$$

Amplifier Specifications

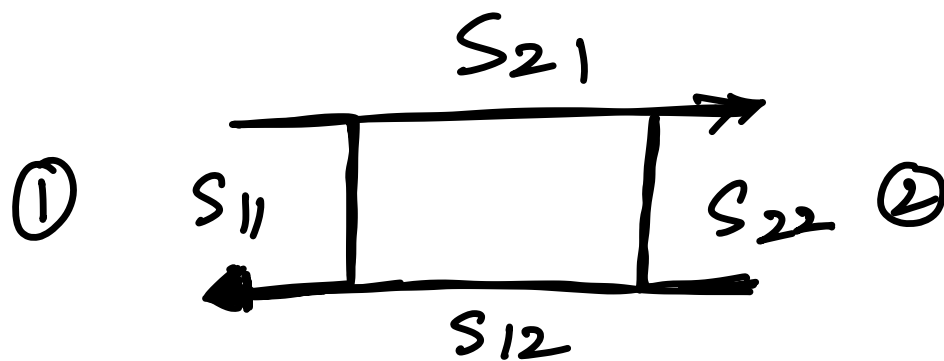- 1) Gain 2) Bandwidth (-3dB)
- 3) Group delay 4) Noise Figure
- 5) Large signal parameters (Compression, Harmonics...)
- 6) P_{oc} 7) Efficiency 8) Stability.



Stability of RF Amplifiers

► $|\Gamma_{in}| > 1$ or $|\Gamma_{out}| > 1$ there is a potential for instability.

► If $|\Gamma_{in}| < 1$ & $|\Gamma_{out}| < 1$ then it is guaranteed to be stable.

Stability Circles

$$\Gamma_{in} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$

$$\Gamma_{out} = S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S}$$

$$|\Gamma_{in}| = 1$$

$$\Rightarrow \left| S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \right| = 1 \quad \text{solve for } \Gamma_L$$

∴ Pozar Sec 12.2

$$\left| \Gamma_L - \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \right| = \left| \frac{S_{12} S_{21}}{|S_{22}|^2 - |\Delta|^2} \right|$$

$\underbrace{\hspace{10em}}_{\text{Center}} \quad \underbrace{\hspace{10em}}_{\text{Radius.}}$


$\xrightarrow{\text{blue}} S_{11} S_{22} - S_{12} S_{21}$

$$C_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2}$$

$$R_L = \left| \frac{S_{12} S_{21}}{|S_{22}|^2 - |\Delta|^2} \right|$$


$$C_s = \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2}$$

$$R_s = \left| \frac{S_{12} S_{21}}{|S_{11}|^2 - |\Delta|^2} \right|$$

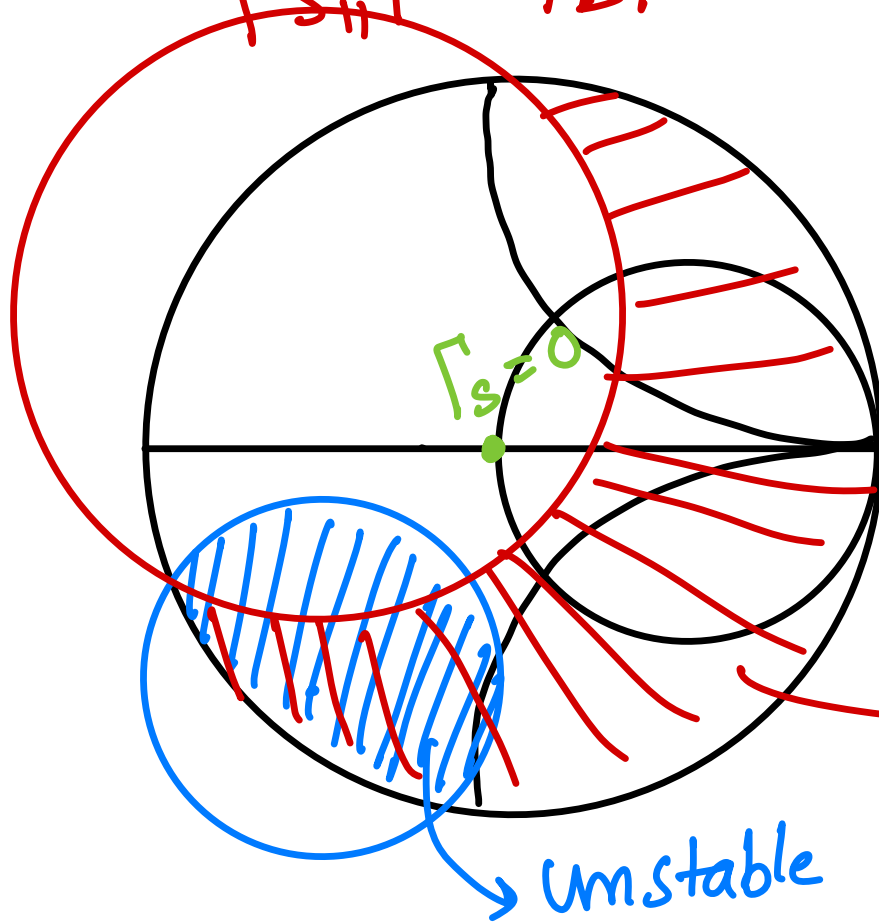

$$|S_{22}| < 1 \\ \Rightarrow |\Gamma_{out}| < 1 \\ \text{when } \Gamma_s = 0$$

→ unstable.

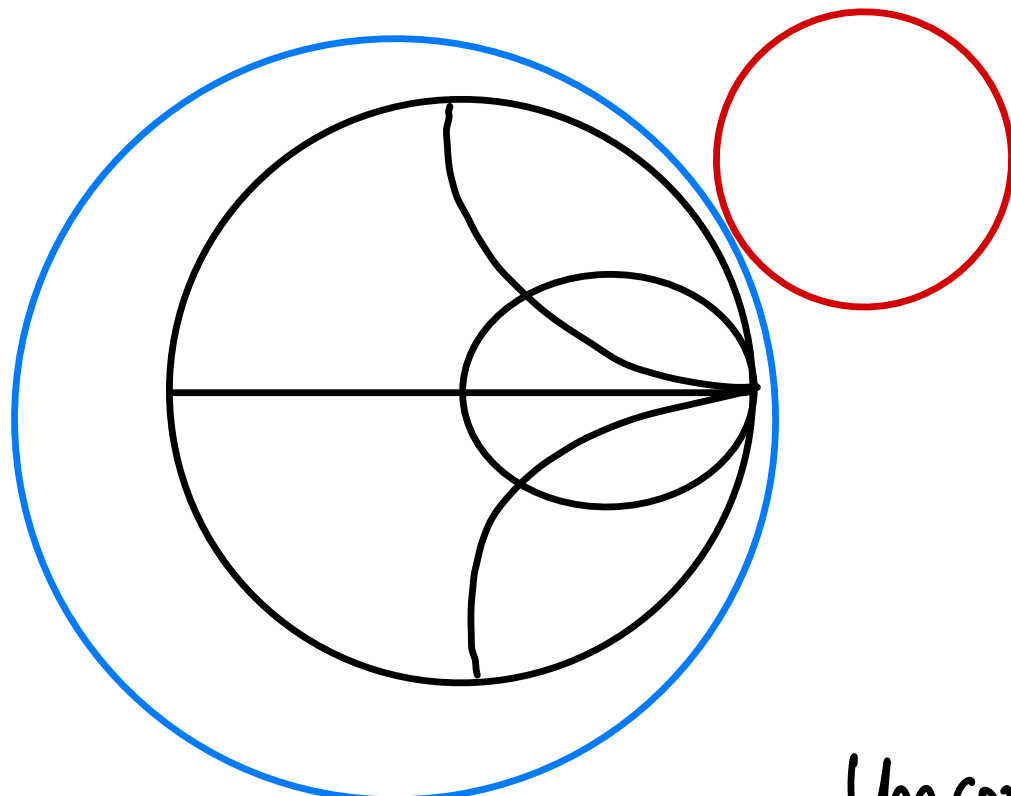

$$|S_{11}| < 1 \\ |S_{22}| < 1$$

$$||C_L| - |R_L|| > 1 \Rightarrow \text{Unconditional Stability.}$$

K-Δ Test

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2}{2|S_{12}S_{21}|} > 1$$

$$|\Delta| = |S_{11}S_{22} - S_{12}S_{21}| < 1$$

μ-Test

$$\mu = \frac{1 - |S_{11}|^2}{|S_{22} - \Delta S_{11}^*| + |S_{12}S_{21}|} > 1$$

$\mu \rightarrow$ is also a measure of stability.

Steps

- ① Measure S-parameters.
- ② K-Δ or μ-test for unconditional stability. } over freq range.
- ③ Plot the source & load stability circles.
- ④ Then proceed with picking Z_s, Z_L .